



ted Pages : 7

TEE - 201

Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2019

Roll No.

0 7 3 0 9 1 3 0 4 8

**B. Tech.**

(SEM. II) EXAMINATION. 2007-08

**ELECTRICAL ENGG.**

Time : 3 Hours]

[Total Marks : 100

Attempt any **four** parts of the following:

4×5=20

(a) An alternating voltage is  $V=100 \sin 100 t$  ;  
find

(i) Amplitude

(ii) Time period and frequency

(iii) Angular velocity

(iv) Form factor

(v) Crest factor.

(b) Determine the following in the circuit shown in  
**Fig 1b.**

(i) The current phasors  $I$ ,  $I_1$  and  $I_2$ .

(ii) Active Power dissipated in the three  
resistive branches.

(iii) Power factor of the circuit.



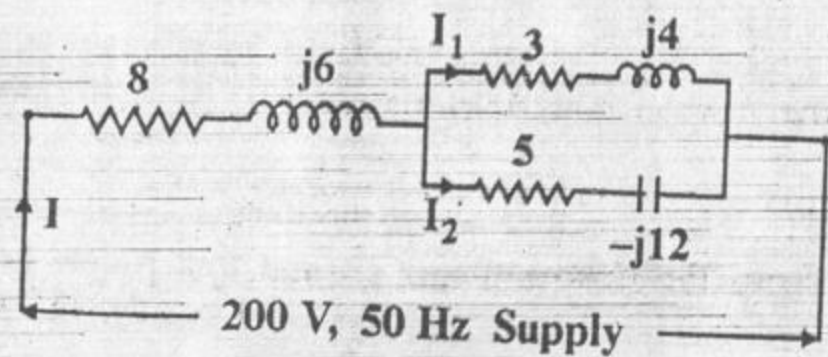


Fig. 1b

Find :

- (i) Magnetic field intensity
- (ii) Reluctance
- (iii) Permeability.

2. Attempt any **four** parts of the following : 4×5=20

- (a) Find the currents in all the resistive branches of the circuit shown in Fig 2.a by

- (i) KVL
- (ii) KCL

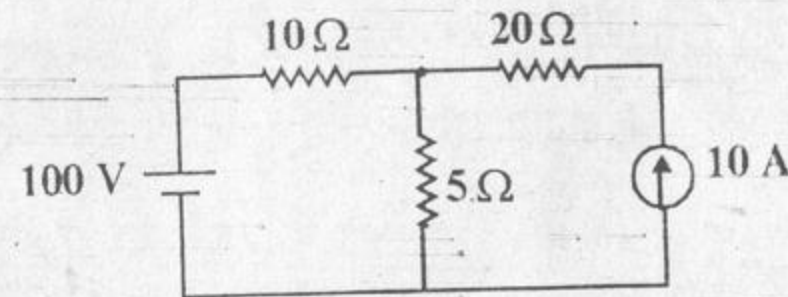


Fig. 2.a

- (b) Determine the value of current through the 5 ohm resistance using Norton's theorem in the circuit shown in fig 2.b. State whether superposition theorem can be applied for the circuit with reasons.

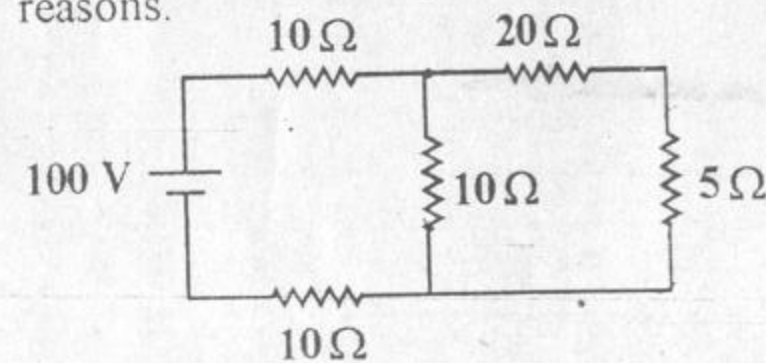


Fig. 2.b

- (c) Explain the concept of bandwidth and quality factor for a series R-L-C circuit. Derive their expressions.


- (d) Establish the analogy between electric and magnetic circuits.

- (e) An effective voltage of 100 V is applied to the parallel combination of two impedances  $\bar{Z}_1 = R_1 + jX_1$  and  $\bar{Z}_2 = R_2 + jX_2$ . Assume that  $R_1 = 3 \Omega$  and  $R_2 = 4 \Omega$  and the magnitude of the two branch currents are same; determine the values of  $X_1$ ,  $X_2$  and the resultant source current.

- (f) A ring of ferromagnetic material has a rectangular cross section. The inner diameter is 7.4 in., the outer diameter is 9 in., and the thickness is 0.8 in. There is a coil of 600 turns wound on the ring. When the coil carries a current of 2.5A, the flux produced in the ring is  $1.2 \times 10^{-3} \text{ Wb}$ .




- (c) In the network shown in **Fig 2.c** find
- The value of  $R_L$  for maximum power dissipation.
  - The value of the maximum power.

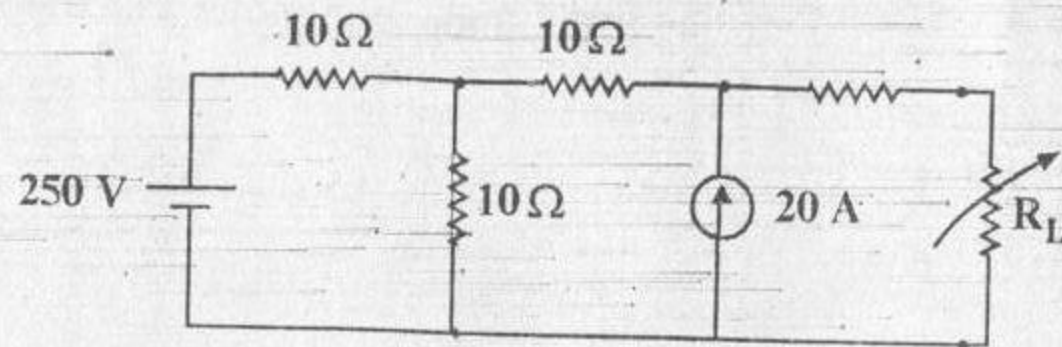

**Fig. 2.c**

- Explain the construction and working principle of a PMMC type instrument. What will it give as output if a half wave rectified ac having peak value of 100 is given as input?
- Explain the construction and working principle of a Moving Iron attraction type instrument. Why is its scale non-uniform?
- In the circuit shown in **fig 2.f**, find the current through the  $6\ \Omega$  resistor using superposition theorem.

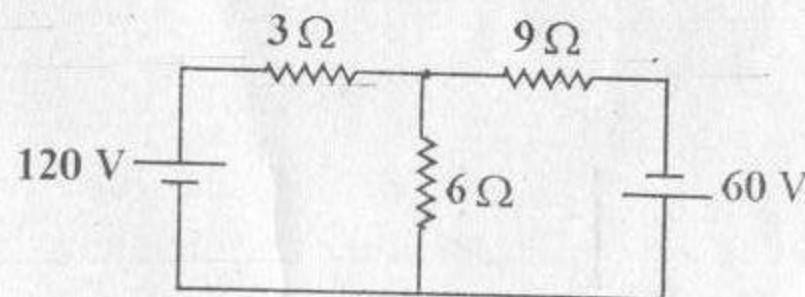

**Fig. 2.f**

**3** Attempt any **two** parts of the following: **2×10=20**

- Derive and explain the two Wattmeter method of measurement of three phase power for a balanced star connected load. How is the three phase power determined? Discuss the variations in readings for different power factors of loads from unity to zero.
- A balanced 3-phase star-connected load of 180 kW taking a leading current of 60 amperes when connected across a 3-phase 440 V, 50 Hz supply. Find the values and nature of the load components and also power factor of the load.
- Draw the phasor diagram of a single phase transformer for leading power factor load.

The efficiency of a 400 kVA, single phase transformer is 98.77% at full load 0.8 power factor and 99.13% at half full load unity power factor.

Find :

- Iron losses at full and half full-loads
- Cu losses at full and half full loads

**4** Attempt any **four** parts of the following: **4×5=20**

- Draw and explain the load characteristics of a DC generator. What is the reason for the difference in the load characteristics for a self and separately excited DC generator?



(b) Derive the EMF equation of a DC generator. What are Lap and Wave windings? Which among them is used for high current and which for high voltage DC generator?

(c) A DC generator (self-excited) fails to build up. Discuss the reasons and remedies for the problem.

(d) Briefly explain the various speed control methods of a DC motor. Which one of them is called constant torque method and why?

(e) A DC shunt motor runs at 600 rpm taking 60 A from a 230 V supply. Armature resistance is 0.2 ohm and field resistance is 115 ohms. Find the speed when the current through the armature is 30A.

(f) Draw and explain the torque-speed, torque-current and speed current characteristics of a DC series motor. Give two applications of the DC motor.

5 Attempt any two parts of the following:  $2 \times 10 = 20$

(a) Derive and draw the torque-slip characteristics of a 3-phase Induction motor. Show, the Breaking and Generating regions explaining the particular values of slips in these two regions.

(b) Explain power flow in a 3-phase Induction Motor. Derive the relationship

$$P_g : P_{\text{mech}} : P_{\text{cu}} = 1 : (1-S) : S$$

Why is the core loss neglected in the rotor circuit of a 3-phase induction motor?

(c) Write short notes on the following :

(i) How the motors generally used in ceiling fans of daily use, are made self starting?

(ii) Rotating magnetic field in a 3-phase induction motor.

(iii) Induction motor as a transformer.